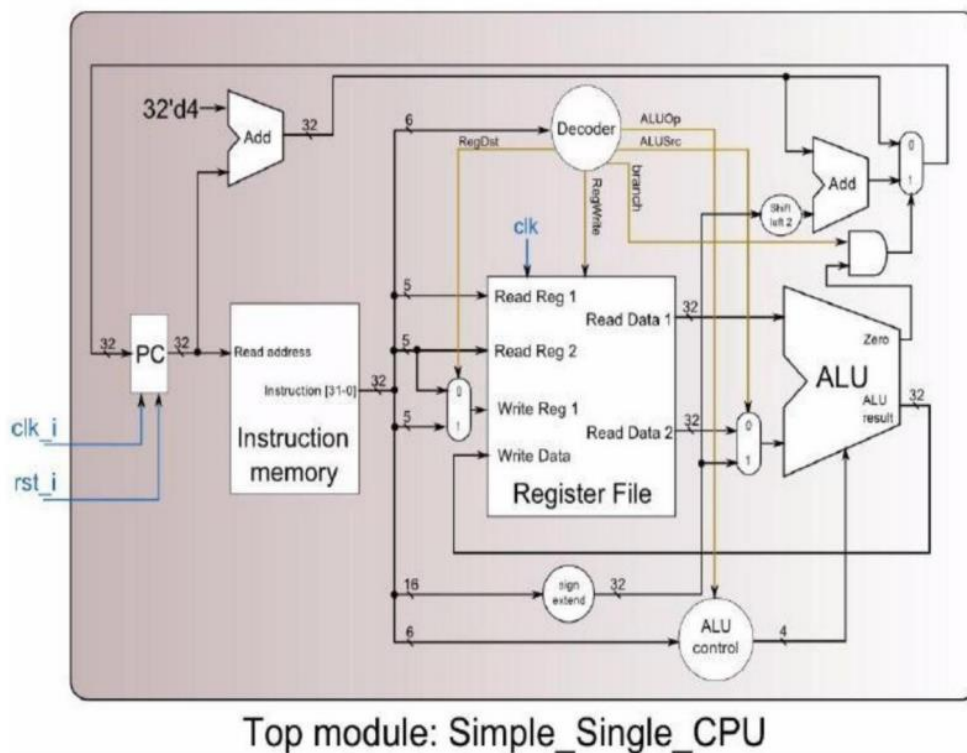


Computer Organization Lab2

Name:邱弘竣

ID:109550136

Architecture diagrams:



- r-type
 - instruction[31:26] is sent to decoder
 - bits are sent into read reg 1 and read reg 2
 - Do the operation in ALU controlled by ALU control
 - the result will be sent to write data
 - $PC = PC + 4$
- addi
 - bits are sent to read reg 1 and sign extend
 - add two numbers from read data 1 and sign extend in ALU
 - the result will be sent to write data
- beq
 - bits are sent to read reg 1 and sign extend
 - subtract two numbers from read data 1 and sign extend in ALU

- if two numbers are equal, then “zero”=1
 - $PC = PC + 4 + (\text{sign extend}) * 4$ (zero=1 and branch =1)
- slti
 - bits are sent to read reg 1 and sign extend
 - compare two numbers from read data 1 and sign extend in ALU
 - if the condition is true, then “zero”=1
 - $PC = PC + 4$


Hardware module analysis:

(explain how the design work and its pros and cons)

- Adder.v
 - add two given numbers
- ALU_Ctrl.v
 - input funt_i and ALUOp_i
 - output ALUCtrl_o to control ALU to do different operations
- ALU.v
 - Given different ctrl_i, ALU can do different operations
- decoder.v
 - input instruction[31:26]
 - output RegWrite_o , ALU_op_o, ALUSrc_o, RegDst_o, Branch_o to control other modules to do different operations
- MUX_2to1.v
 - Given 0 or 1
 - do the selected things
- Shift_Left_Two_32.v
 - input a 32-bit data
 - output the data multiplied by 4
- Sign_Extend.v
 - convert 16-bit data to 32-bit
- Simple_Single_CPU.v
 - connect all the modules to implement all the MIPS code
- pros : easy to implement.
- cons : It's very slow because it can only do one operation in one time.

Finished part:

(show the screenshot of the simulation result and waveform, and explain it)

 

Part1

```
2
r0= 0
r1= 10
r2= 4
r3= 0
r4= 0
r5= 6
r6= 0
r7= 0
r8= 0
r9= 0
r10= 0
r11= 0
r12= 0
```

Part2

```

      2
r0=    0
r1=    1
r2=    0
r3=    0
r4=    0
r5=    0
r6=    0
r7=   14
r8=    0
r9=   15
r10=   0
r11=   0
r12=   0

```

All the result are the same as CO_Lab_2.pdf

Problems you met and solutions:

- In the begining, I didn't know what Decoder is. I tried to find out the answer in Teacher's ppt and .txt in our project. Instruction[31:26] is the input of Decoder, deciding which type of operation is now chosen. Then I checked the code in CO_P2_test_data1.txt and compared it to CO_Lab_2.pdf. I finally understood how Decoder works.
- There are too many modules this time. In the begining I didn't how to do it because Simple_Single_CPU.v was almost empty. Then I checked the diagram in CO_Lab_2.pdf and then I understood how are these modules connect with one another.

Summary:

Indeed, I'm not famiililar with verilog at all. However, after these labs, I think I understand verilog much more than before. Although software programming is still easier for me, I will try to improve myself in the future courses.